

浙江大学

本科实验报告

课程名称：计算机组成

姓名：曾一欣

学院：竺可桢学院

班级：求是科学班（计算机科学与技术）

专业：计算机科学与技术

学号：3180105144

指导老师：姜晓红

2020.7.9

浙江大学实验报告

课程名称：计算机组成 实验类型：综合

实验项目名称：bonus mul/div/中断

学生姓名：曾一欣 专业：计算机科学与技术 学号：3180105144

同组学生姓名：None 指导老师：姜晓红


实验地点：无 实验日期：2020年7月9日

一、实验目的和要求


1. 设计乘法器和除法器，设计mul和div语句执行的datapath和ctrl
2. 设计简单的中断方式，实现eret指令

二、实验内容和原理


Decomposability of computer systems

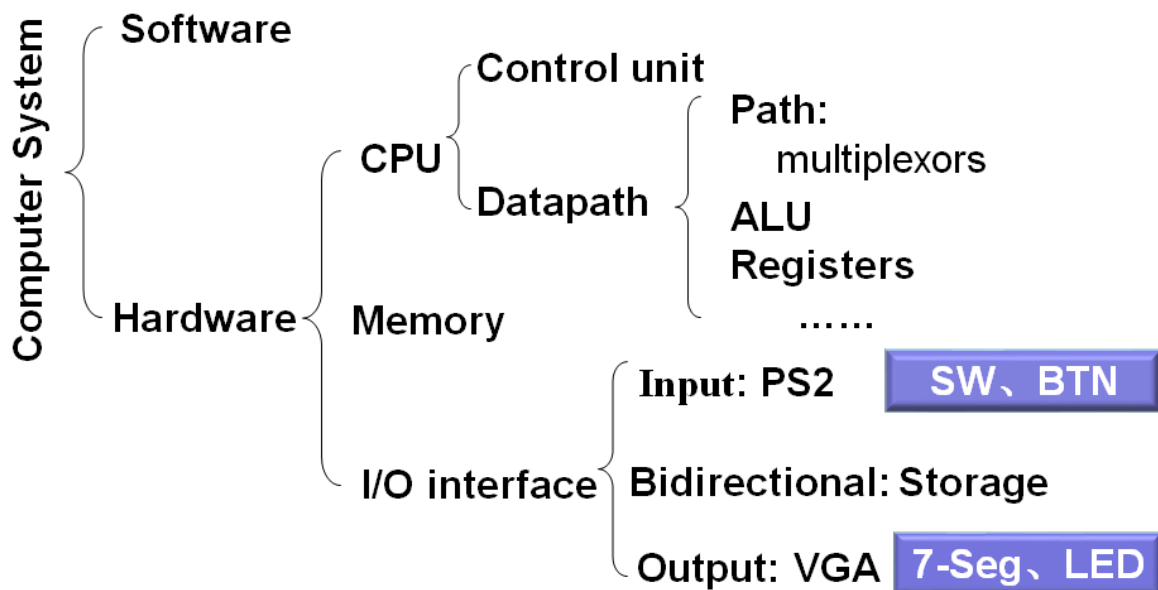


Digital circuit

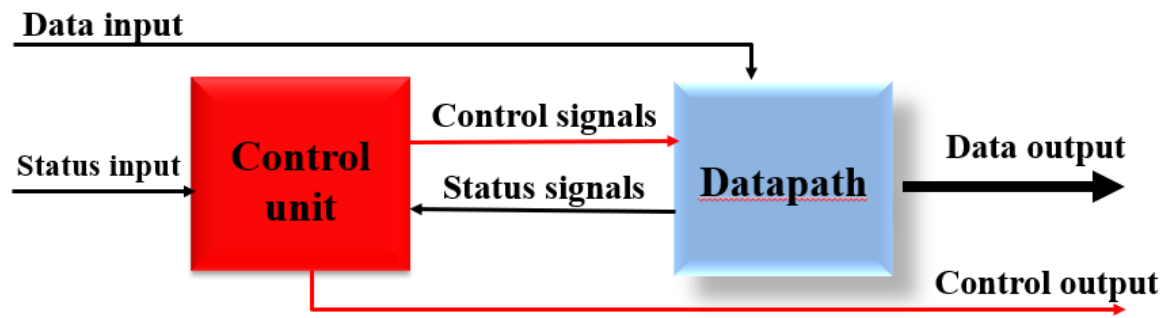

DataPath

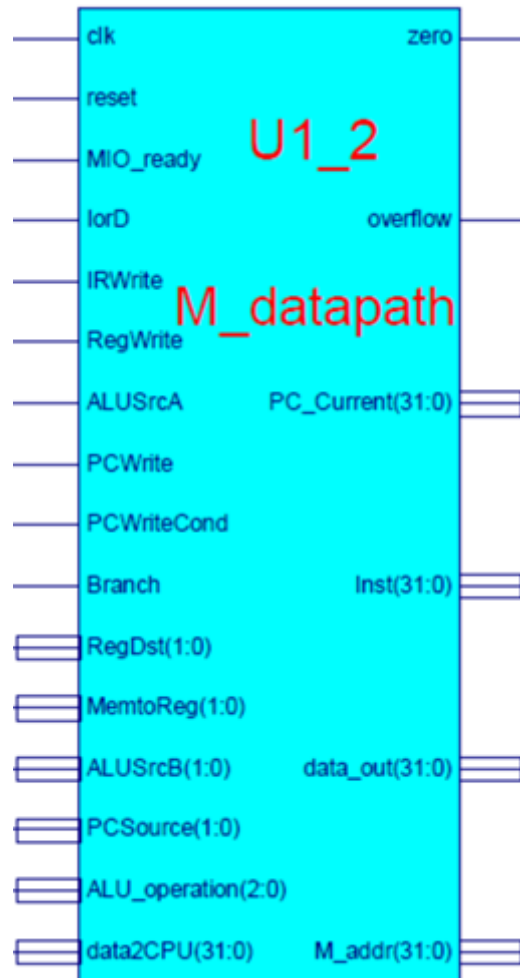


Controller

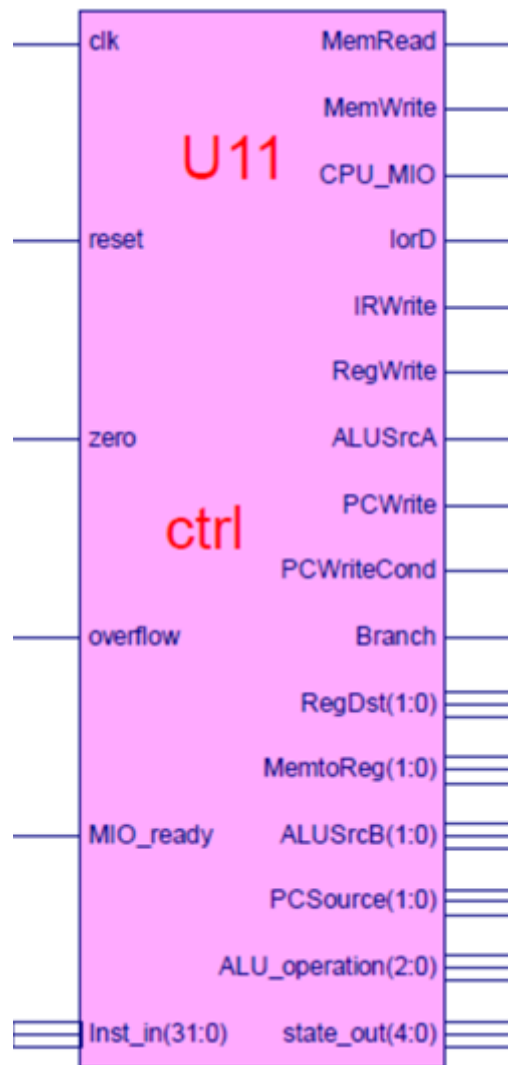

ALU


use the same module ALU in SCPU

| ALU Control Lines | Function | note |
|-------------------|-------------------------|------|
| 000 | And | 兼容 |
| 001 | Or | 兼容 |
| 010 | Add | 兼容 |
| 110 | Sub | 兼容 |
| 111 | Set on less than | |
| 100 | nor | 扩展 |
| 101 | srl | 扩展 |
| 011 | xor | 扩展 |

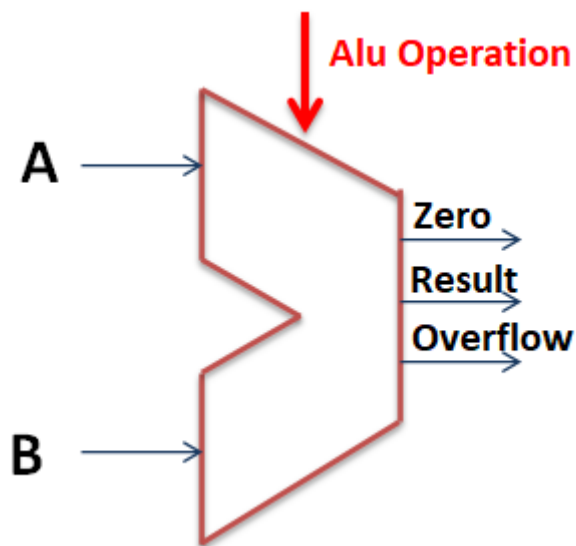


Register file


use the same module in SCPU

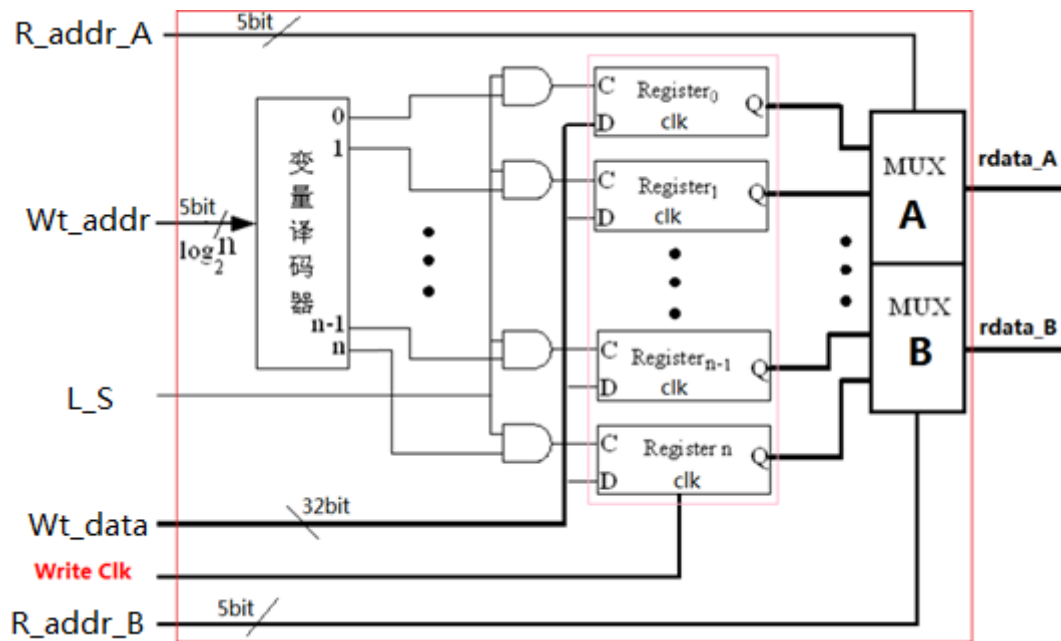


mul

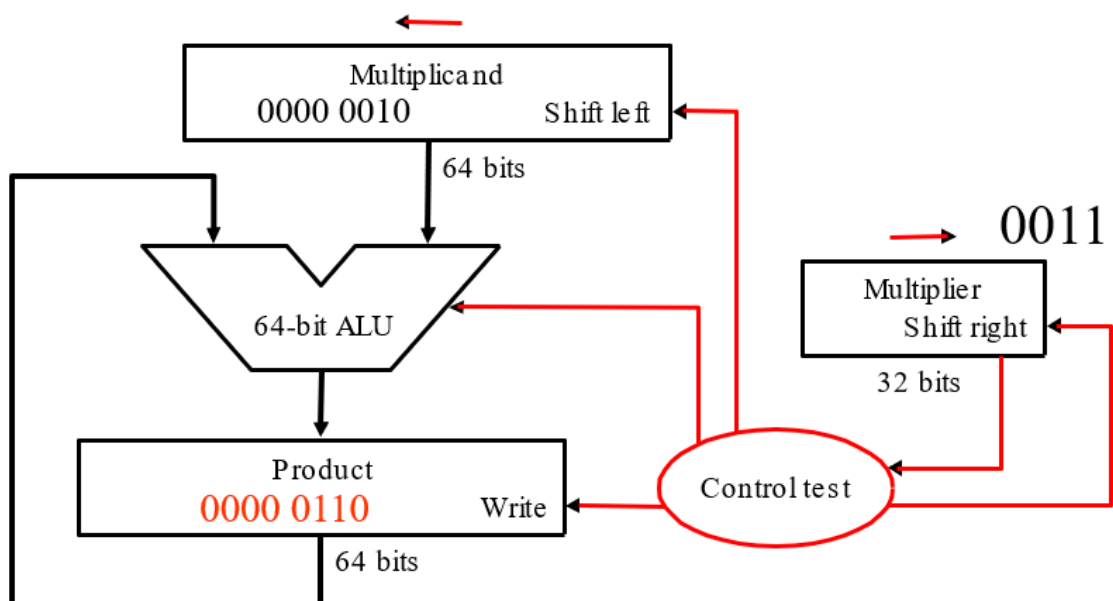


div

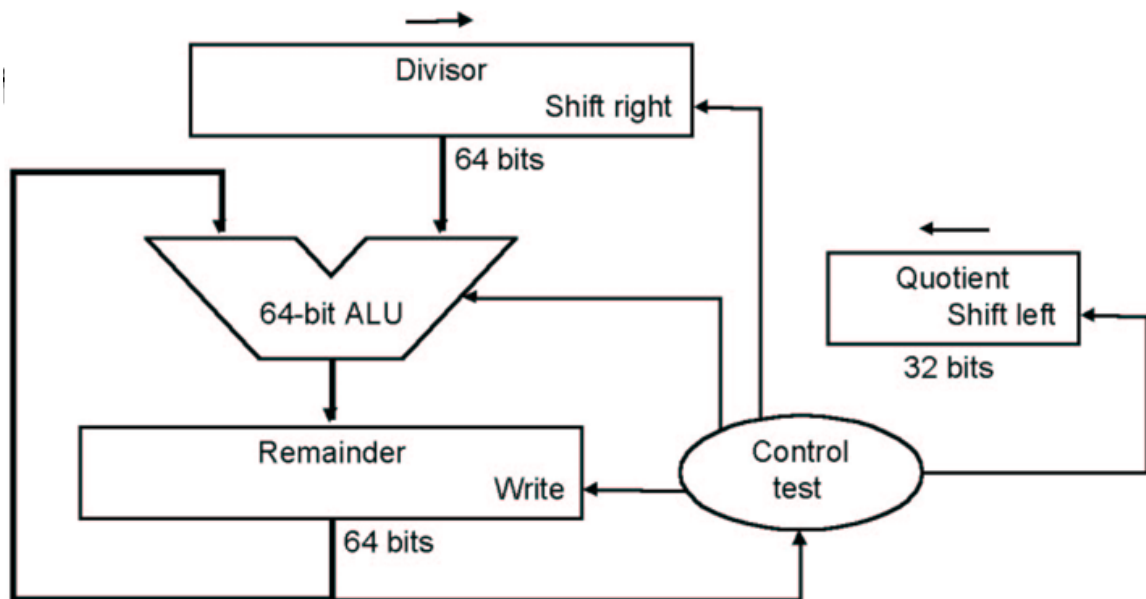

中断

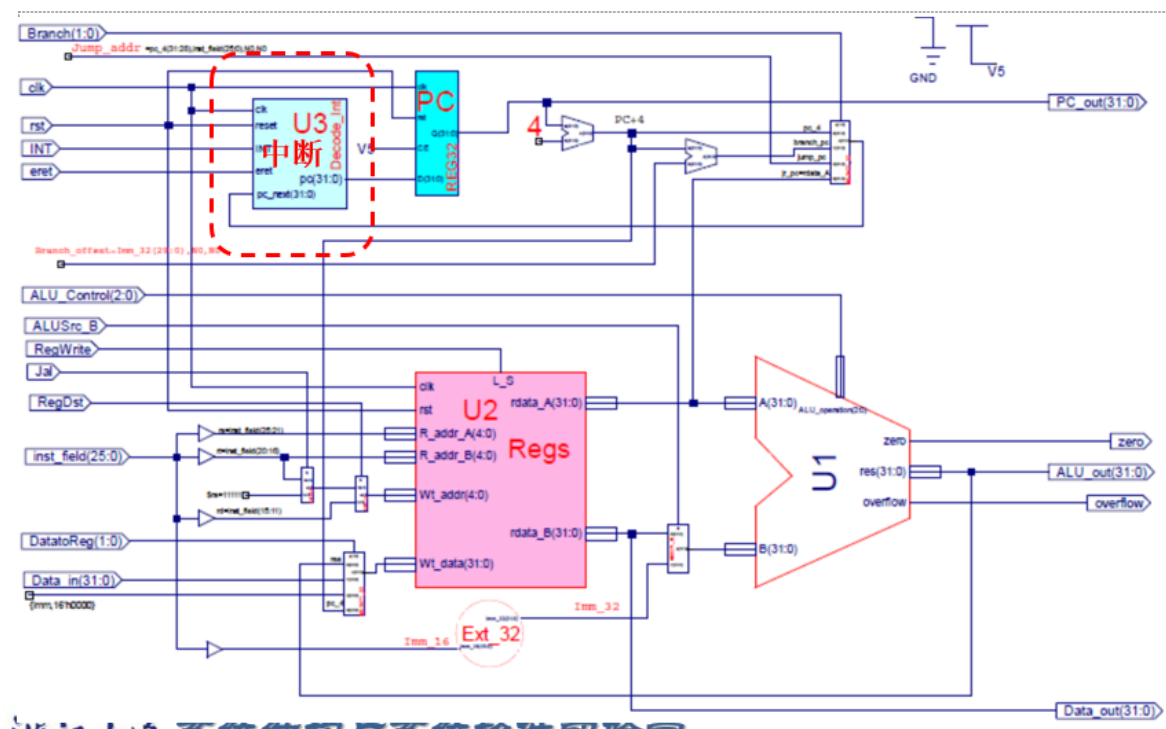

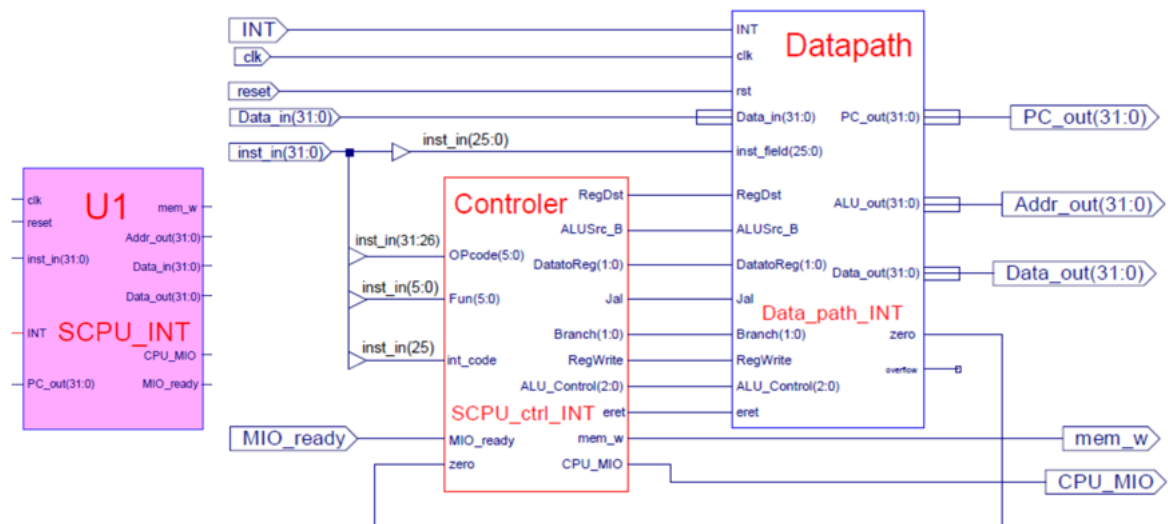

三、实验过程和数据记录及结果分析

Search for the structure of mul, div and eret

mul

multu、mult, mul 指令

| 31 | 26 | 25 | 21 | 20 | 16 | 15 | 11 | 10 | 6 | 5 | 0 | |
|--------------------|----|----|-------|-------|-------|-------|-------|-------|-------|-------|-----------------|---------|
| SPECIAL2 011100 | rs | rt | rd | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | MUL 000010 | mul指令 |
| SPECIAL 000000 | rs | rt | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | MULT 011000 | mult指令 |
| SPECIAL 000000 | rs | rt | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | MULTU 011001 | multu指令 |

- 当指令码为SPECIAL2，功能码为6b000010时，表示mul指令，乘法运算。

指令用法为：mul rd, rs, st。

指令作用为： $rd \leftarrow rs \times rt$ ，将地址为rs的通用寄存器的值与地址为rt的通用寄存器的值作为有符号数相乘，乘法结果的低32bit保存到地址为rd的通用寄存器中。

div

div、divu指令

| 31 | 26 | 25 | 21 | 20 | 16 | 15 | 11 | 10 | 6 | 5 | 0 | |
|-------------------|----|----|-------|-------|-------|-------|-------|-------|-------|-------|----------------|--------|
| SPECIAL 000000 | rs | rt | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | DIV 011010 | div指令 |
| SPECIAL 000000 | rs | rt | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | 00000 | DIVU 011011 | divu指令 |

- 当功能码是6b011010时，表示是div指令，有符号除法运算。

指令用法为：div rs, rt。

指令作用为：(HI, LO) \leftarrow rs/rt，将地址为rs的通用寄存器的值，与地址为rt的通用寄存器的值，作为有符号数进行除法运算，将商保存到寄存器LO，余数保存到寄存器HI。

eret

■ eret

- PC \leftarrow EPC; (CP0的Cause和Status寄存器有变化)

| Op=6bit | 1 | 19bit | FUN |
|---------|---|-------------------------|--------|
| 0x0 | 1 | 000 0000 0000 0000 0000 | 011000 |

Modules

decoder INT

```

module Decoder_INT(
    input clk,
    input reset,
    input INT,
    input eret,
    input [31:0] pc_next,
    output reg [31:0] pc
);

reg doing = 0, cando = 1, newint = 0;
reg [31:0] EPC;

always @(posedge clk or posedge reset)
begin
    if (reset)
        begin
            doing <= 0;
            cando <= 1;
            EPC <= 0;
        end
    else if (cando & newint)
        begin
            doing <= 1;
            cando <= 0;
            EPC <= pc_next;
        end
    else begin
        doing <= 0;
        if (eret) cando <= 1;
    end
end

wire clr;
assign clr = reset | doing;
always @(posedge INT or posedge clr)
begin
    if (clr) newint <= 0;
    else newint <= 1;
end

```




```

end
always @*
begin
    if (reset)
        pc <= 32'h00000000;
    else if (cando & newint) pc <= 32'h00000004;
    else if (eret) pc <= EPC;
    else pc <= pc_next;
end
endmodule

```

change of datapath


connected to PC register

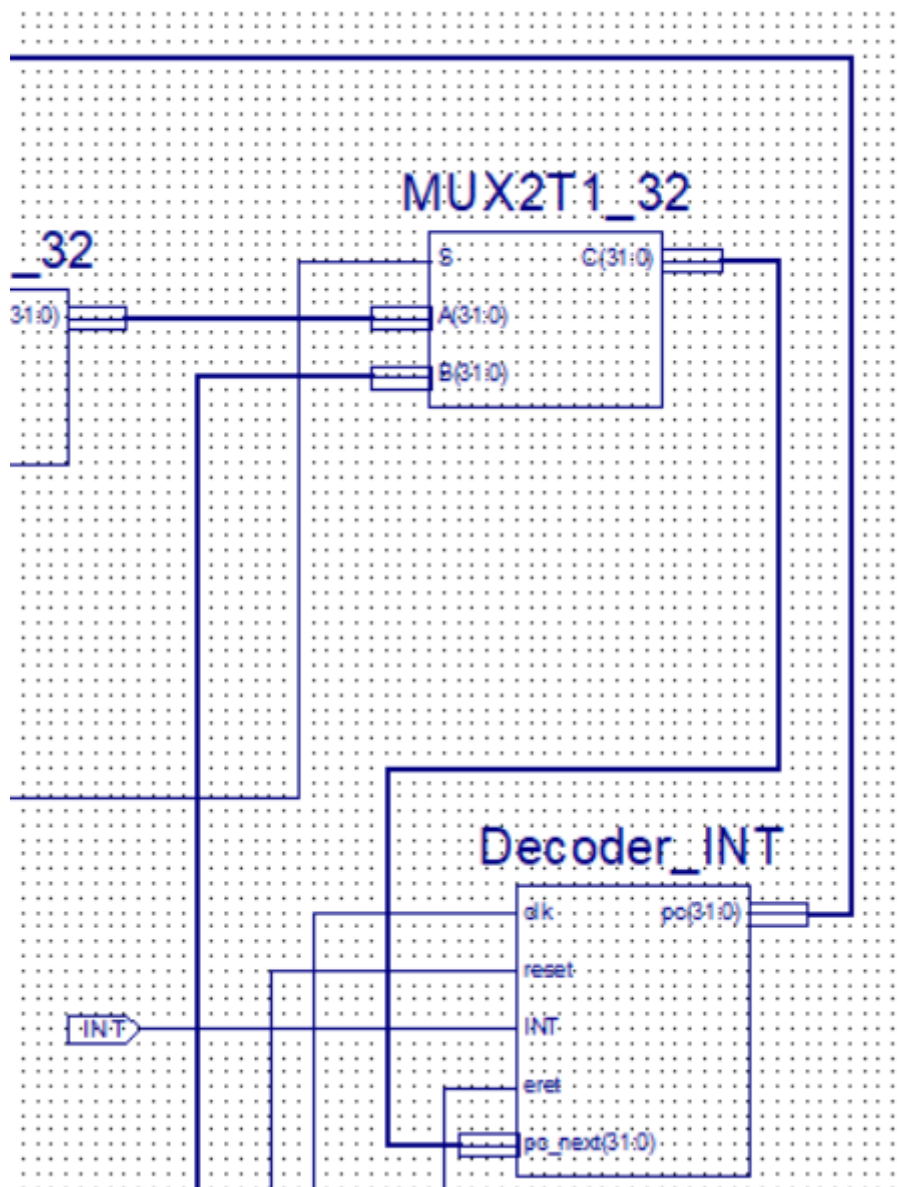

change of ctrl and top

ctrl: add "assign eret=(opcode==6'b010000&&func==6'b011000)?1:0;"

top: connect INT to SW_OK[1]

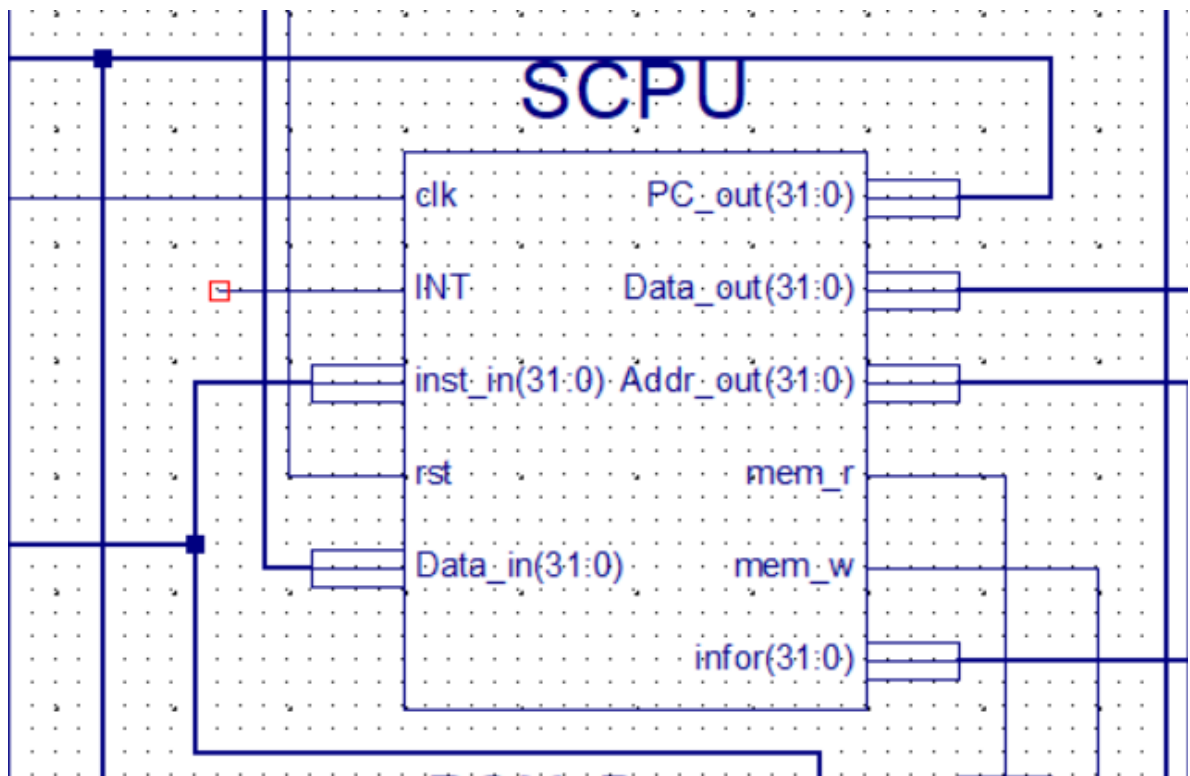

mul

```

module mul(
    input clk,rst,
    input start,
    input [31:0] a,
    input [31:0] b,
    output done,
    output [31:0] yji,
    output [31:0] test
);
reg[31:0] temp_c;
reg[31:0] temp_b;
reg[5:0] i;
reg done_r;

always @(posedge clk or posedge rst)begin
    if(rst) i = 6'd0;
    else if(start&& i<6'd33) i = i+1'b1;
    else i = 6'd0;
end

always @(posedge clk or posedge rst)
    if(rst) done_r = 1'b0;
    else if(i == 6'd32) done_r = 1'b1;
    else if(i == 6'd33) done_r = 1'b0;
assign done = done_r;

always @ (posedge clk or posedge rst)begin
    if(rst) begin
        temp_c = 64'h0;
        temp_b = 64'h0;
    end
    else if(start) begin
        if(i == 6'd0) begin

```

```

        temp_c = 0;
        temp_b = b;
    end
    else begin
        temp_c = temp_c << 1;
        if(temp_b[31]==1) temp_c = temp_c + a;
        else temp_c = temp_c;
        temp_b=temp_b<<1;
    end
end
end

assign yji = temp_c[31:0];
assign test=temp_b;

endmodule

```

div

```

module div(
    input clk,rst,
    input start,
    input [31:0] a,
    input [31:0] b,
    output done,
    output [31:0] yshang,
    output [31:0] yyushu
);
    reg[63:0] temp_a;
    reg[63:0] temp_b;
    reg[5:0] i;
    reg done_r;

    always @(posedge clk or posedge rst)begin
        if(rst) i = 6'd0;
        else if(start&& i<6'd33) i = i+1'b1;
        else i = 6'd0;
    end

    always @(posedge clk or posedge rst)
        if(rst) done_r = 1'b0;
        else if(i == 6'd32) done_r = 1'b1;
        else if(i == 6'd33) done_r = 1'b0;
    assign done = done_r;

    always @ (posedge clk or posedge rst)begin
        if(rst) begin
            temp_a = 64'h0;
            temp_b = 64'h0;
        end
        else if(start) begin
            if(i == 6'd0) begin
                temp_a = {32'h00000000,a};
                temp_b = {b,32'h00000000};
            end
            else begin
                temp_a = temp_a << 1;

```

```

        if(temp_a >= temp_b) temp_a = temp_a - temp_b + 1'b1;
        else temp_a = temp_a;
        end
    end
end

assign yshang = temp_a[31:0];
assign yyushu = temp_a[63:32];
endmodule

```

change of datapath

```

REG32  ALUREG (.CE(V5),
               .clk(clk),
               .D(mul?mul_out:res[31:0]),
               .rst(NO),
               .Q(ALU_out[31:0]));

mul mul1(.clk(clk),.rst(reset),
        .start(mul),
        .a(RdataA),
        .b(data_out),
        .done(mul_done),
        .yji(mul_out),
        .test());

div divv(.clk(clk),.rst(reset),
        .start(div),
        .a(RdataA),
        .b(data_out),
        .done(div_done),
        .yshang(div_out1),
        .yyushu(div_out2));

//assign test3=div_out1;
//assign test2=div_out2;

REG32  LO (.CE(wdiv),
          .clk(clk),
          .D(div_out1),
          .rst(NO),
          .Q(test3));

REG32  HI (.CE(wdiv),
          .clk(clk),
          .D(div_out2),
          .rst(NO),
          .Q(test2));

```

change of ctrl

```

ID: begin case (Inst_in[31:26])
    6'b000000: begin
        case(Inst_in[5:0])
            6'b000000: state<=EX_shift;
            6'b000010: state<=EX_shift;

```

```

        6'b011010: state<=EX_div; //div
        6'b001000: state<=EX_jr; //jr
        default:state <= EX_R; //R-type OP
    endcase
end
6'b011100: state <= EX_mul; //mul
6'b000010: state <= Exe_J; // j
6'b000011: state <= EX_JAL; // jal
6'b000100: state <= EX_beq; // beq
6'b000101: state <= EX_bne; // bne
6'b001000: state <= EX_I; // addi
6'b001010: state <= EX_I; // slti
6'b001100: state <= EX_I; // andi
6'b001101: state <= EX_I; // ori
6'b001110: state <= EX_I; // xori
6'b001111: state <= Lui_WB; // lui
6'b100011: state <= EX_Mem; // lw
6'b101011: state <= EX_Mem; // sw
default: state <= Error;
endcase
end
EX_mul: begin if(mul_done) state<=WB_mul;
            else state<=state;
        end
EX_div: begin if ( div_done )state<=IF;
            else state<=state;
        end
WB_mul: state<=IF;


```

```

EX_div: begin ` CPU_ctrl_signals = 17'b00000000001000000; Branch=0; shift=0;
div=1; mul=0; wdiv=1; end
EX_mul: begin ` CPU_ctrl_signals = 17'b00000000001000000; Branch=0; shift=0;
div=0; mul=1; wdiv=0; end
WB_mul: begin ` CPU_ctrl_signals = value7; Branch=0; shift=0; div=0; mul=1;
wdiv=0; end

```

change of top

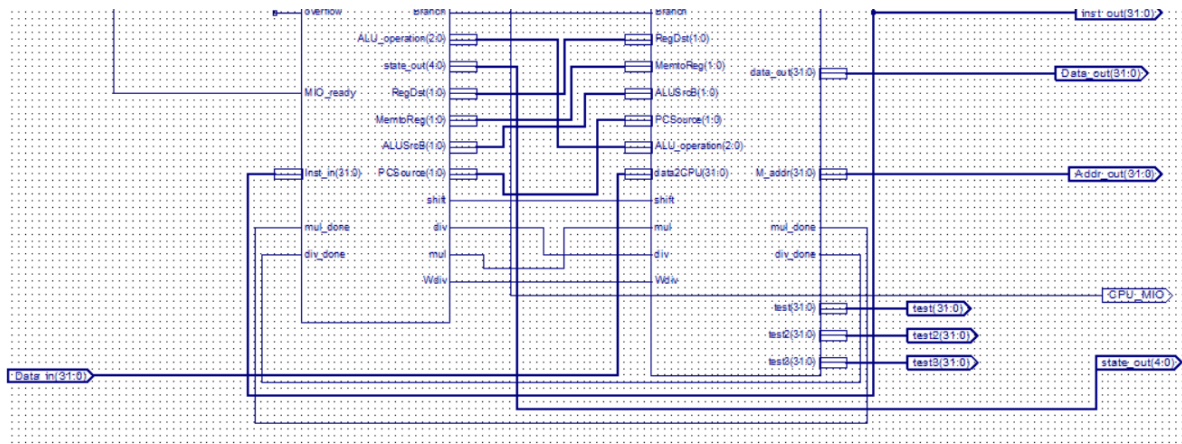

四、讨论与心得

In this experiment we are asked to realize mul/div and simple INT. With the convenience of verilog we can construct mul/div easily by coding instead of drawing schematic. And for INT, the main purpose is to realize eret instruction. I connect INT signal to SW_OK(1) so that we can stop the CPU using switch. And for the test coe, it will jump to a series of I-type instructions and finally fall in to eret.

This is the end of experiments in this course. I've been to the lab in school and debug all my projects. After finishing all the debugging, go back and see the reports before, I can really find many errors and finally careless mistakes. What's more, now I have a better understanding of top, datapath, ctrl and other modules instead of simply copy them from PPT. Then I realize the meaning of doing experiments offline.